

resultados P3_electronica

Jesús Brandon Villanueva Rivas

September 2026

1 Resultados

Dados los datos de la tabla 1 y los datos simulados en Kicad se construyo la gráfica ??

Table 1: Caracterización del diodo 1N4007.

V_S [V]	V_D [V]	V_R [V]	I_D [mA]
0.0	0.0000	0.000	0.00
0.1	0.1465	0.000	0.00
0.2	0.2149	0.000	0.00
0.3	0.3102	0.000	0.00
0.4	0.4170	0.000	0.01
0.5	0.4900	0.010	0.13
0.6	0.5450	0.055	0.53
0.7	0.5700	0.130	0.73
0.8	0.5880	0.212	1.02
0.9	0.6130	0.287	1.33
1.0	0.6210	0.379	1.87
1.1	0.6280	0.472	2.12
1.2	0.6390	0.561	2.62
1.3	0.6450	0.655	3.12
1.4	0.6510	0.749	3.56
1.5	0.6590	0.841	3.92
1.6	0.6620	0.938	4.16
1.7	0.6670	1.033	4.78
1.8	0.6700	1.130	5.13
1.9	0.6740	1.226	5.51
2.0	0.6770	1.323	5.98
2.1	0.6800	1.420	6.29
2.2	0.6830	1.517	6.77
2.3	0.6860	1.614	7.18
2.4	0.6890	1.711	7.68
2.5	0.6910	1.809	8.06
2.6	0.6950	1.905	8.41
2.7	0.6970	2.003	9.14
2.8	0.6980	2.102	9.65
2.9	0.7000	2.200	9.94
3.0	0.7020	2.298	10.34
3.1	0.7020	2.398	10.64
3.2	0.7030	2.497	11.04
3.3	0.7050	2.595	11.43
3.4	0.7070	2.693	12.04
3.5	0.7080	2.792	12.31
3.6	0.7100	2.890	12.73
3.7	0.7120	2.988	13.39
3.8	0.7130	3.087	13.79
3.9	0.7140	3.186	14.13
4.0	0.7160	3.284	14.50
4.1	0.7170	3.383	15.09
4.2	0.7190	3.481	15.51
4.3	0.7200	3.580	15.92
4.4	0.7210	3.679	16.33
4.5	0.7220	3.778	16.71
4.6	0.7240	3.876	17.44
4.7	0.7240	3.976	17.80
4.8	0.7250	4.075	18.22
4.9	0.7270	4.173	18.84
5.0	0.7280	4.272	19.30